




# Losses in converters

Thursday, March 18, 2021 9:24 AM

→ There are no ideal elements.

→ Let us model a practical inductor.

It only include copper loss

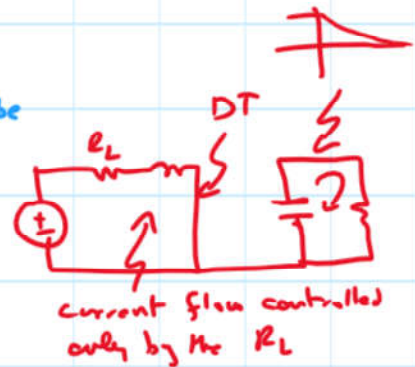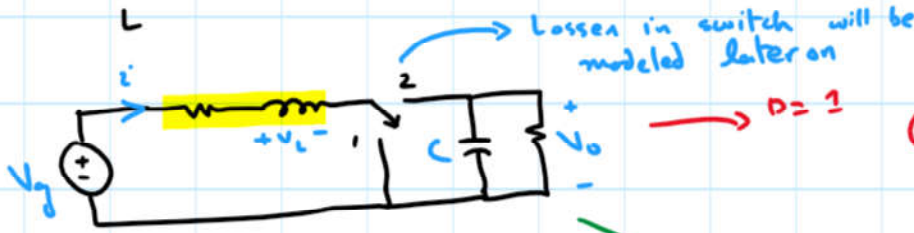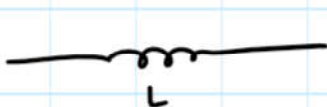

$$V_L(t) = V_g - i(t)R_L$$

$$i_c(t) = \frac{-v(t)}{R}$$



$$V_L(t) = V_g - i(t)R_L - v(t)$$

$$i_c(t) = i(t) - \frac{v(t)}{R}$$

Apply the SRA.

$$V_L(t) = V_g - IR_L$$

$$i_c(t) = -\frac{V}{R}$$

$$V_L(t) = V_g - IR_L - V$$

$$i_c(t) = I - \frac{V}{R}$$

Volt-sec balance through  $V_L(t)$  waveform

$$\langle V_L(t) \rangle = DT_s(V_g - IR_L) + D'T_s(V_g - IR_L - V) = 0$$

For steady state it is zero


$$0 = \underbrace{V_g}_{\text{g/p}} - \underbrace{IR_L}_{\text{unknown}} - \underbrace{D'V}_{\text{o/p}} \quad \text{--- (A)}$$

To solve (A) capacitor charge-sec balance is used

$$\langle i_c(t) \rangle = DT_s(-V/R) + D'T_s(I - V/R) = 0$$

$$0 = D'I - V/R \quad \text{--- (B)}$$

using (A) & (B)

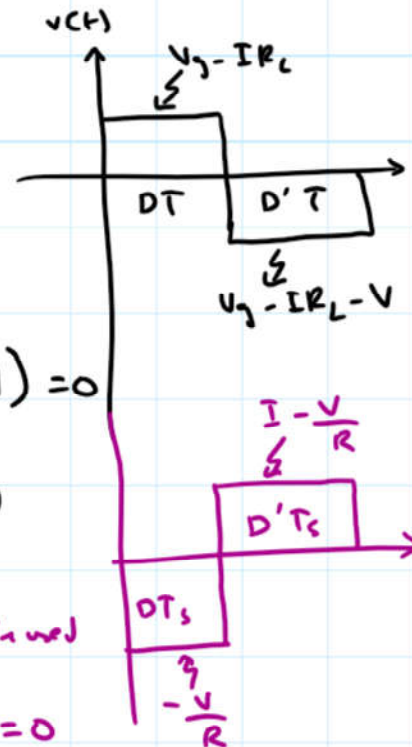

(C)


using (A) & (B)

$$m(D) = \frac{V}{V_g} = \frac{1}{D'} \left[ 1 + \frac{R_L}{D'^2 R} \right] \quad \text{--- (C)}$$

plot  $m(D)$  as a function of  $D$  and  $R_L/R$

E.g. C

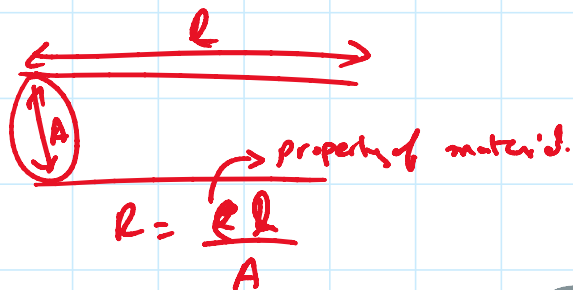- if  $R_L = 0$  then  $V/V_g = \frac{1}{D'} = \frac{1}{1-D}$  and it shows ideal Buck converter
- if  $R_L \ll D'^2 R$  then  $\frac{V}{V_g} \approx \frac{1}{D'}$
- if  $R_L > D'^2 R$  then  $\frac{V}{V_g}$  is reduced.
- At  $D=1$  the  $m(D)$  tends to zero.




$A \uparrow$  winding space occupy  $\uparrow$   
 larger core  $\uparrow$  power density  $\downarrow$

Let us derive (C) using DC Transformer

we need (A) and (B)

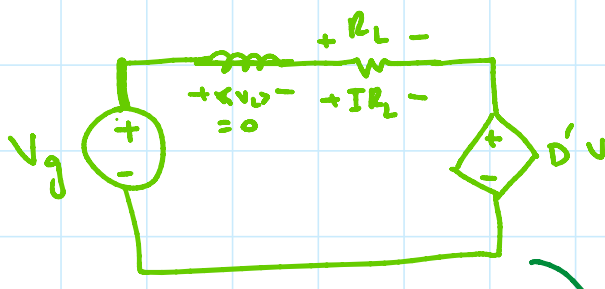
(A)  $\rightarrow V_g - I R_L - D' V = 0 = \langle v_L \rangle$


- $V_g$ : i/p voltage, independent voltage source
- $I R_L$ : voltage drop, modeled using  $R_L$
- $D' V$ : o/p voltage, controlling parameter, modeled as a dependent source.



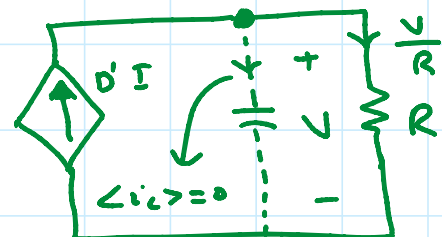(B)  $\rightarrow D' I - \frac{V}{R} = 0 = \langle i_C \rangle$


- $D' I$ : controlled variable current, dependent source
- $\frac{V}{R}$ : capacitor current = 0



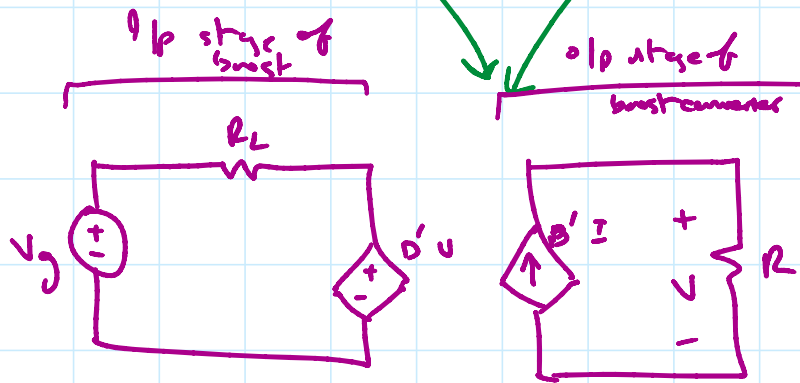

$$1: D(0)$$

$$m(1): 1$$

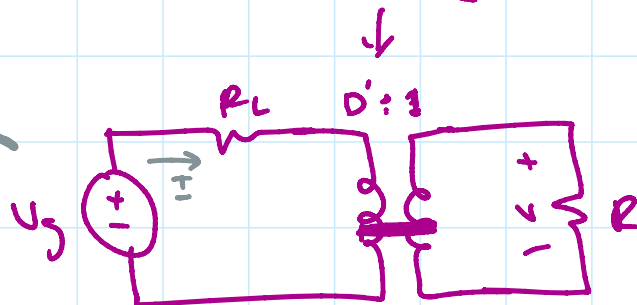

$$\frac{N_p}{N_s} = \frac{V_p}{V_s}$$

$$D':1 = \frac{V_p}{V_s}$$

$$V_s = \frac{V_p}{D'}$$

$$\eta = ?$$

$$P_{in} = V_g I$$

$$P_o = V D' I$$

$$\eta = \frac{V D' I}{V_g I}$$

$$= \frac{V}{V_g} D'$$

putting value of V

$$\eta = \frac{1}{1 + \frac{R_L}{D'^2 R}}$$


Matlab plotting

(E)

Transfer primary side to the sec side.

$$V_g \xrightarrow{\text{sec}} \frac{V_g}{D'}$$
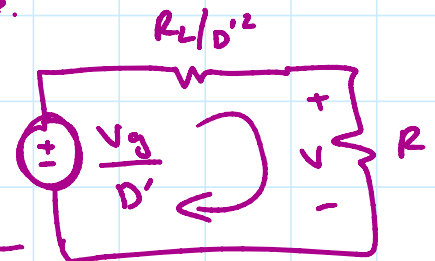
$$R_L \xrightarrow{\text{sec}} R_L / D'^2$$



$$V = \frac{V_g}{D'} \left( \frac{R}{R + \frac{R_L}{D'^2}} \right) \quad \left. \vphantom{\frac{V_g}{D'}} \right\} V_{DR}$$

$$\frac{V}{V_g} = \frac{1}{D'} \frac{1}{1 + \frac{R_L}{D'^2 R}}$$

(D)

Ey (C) and (D) are same.

plot eq (C) & (E) in matlab with addition to different ratio of  $\frac{R_L}{R}$  given in the book